



Question 7. The values of current  $I$  flowing in a given resistor for the corresponding values of potential difference  $V$  across the resistor are given below:

$I$ (amperes)	0.5	1.0	2.0	3.0	4.0
$V$ (volts)	1.6	3.4	6.7	10.2	13.2


Plot a graph between  $V$  and  $I$  and calculate the resistance of that resistor.

Answer:

The plot between voltage and current is called IV characteristic. The voltage is plotted on x-axis and current is plotted on y-axis. The values of the current for different values of the voltage are shown in the given table.

$I$ (amperes)	0.5	1.0	2.0	3.0	4.0
$V$ (volts)	1.6	3.4	6.7	10.2	13.2

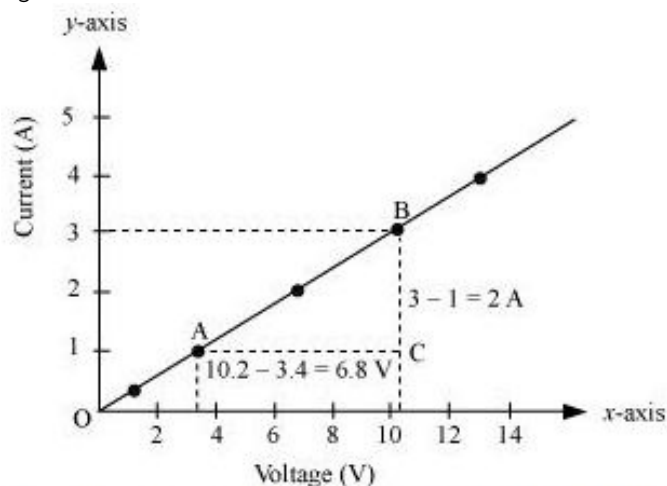The IV characteristic of the given resistor is plotted in the following figure.



The slope of the line gives the value of resistance ( $R$ ) as,

$$\text{Slope} = \frac{1}{R} = \frac{BC}{AC} = \frac{2}{6.8}$$

$$R = \frac{6.8}{2} = 3.4 \, \Omega$$

Therefore, the resistance of the resistor is  $3.4 \, \Omega$ .

Question 8. When a 12 V battery is connected across an unknown resistor, there is a current of 2.5 mA in the circuit. Find the value of

the resistance of the resistor.

Answer:

Resistance ( $R$ ) of a resistor is given by Ohm's law as,

$$V = IR$$

$$R = \frac{V}{I}$$

Where,

Potential difference,  $V = 12 \text{ V}$

Current in the circuit,  $I = 2.5 \text{ mA} = 2.5 \times 10^{-3} \text{ A}$

$$R = \frac{12}{2.5 \times 10^{-3}} = 4.8 \times 10^3 \text{ } \Omega = 4.8 \text{ k}\Omega$$

Therefore, the resistance of the resistor is  $4.8 \text{ k}\Omega$ .

Question 9. A battery of  $9 \text{ V}$  is connected in series with resistors of  $0.2 \text{ ohm}$ ,  $0.3 \text{ ohm}$ ,  $0.4 \text{ ohm}$ ,  $0.5 \text{ ohm}$  and  $12 \text{ ohm}$ , respectively. How much current would flow through the  $12 \text{ ohm}$  resistor?

Answer:

There is no current division occurring in a series circuit. Current flow through the component is the same, given by Ohm's law as

$$V = IR$$

$$I = \frac{V}{R}$$

Where,

$R$  is the equivalent resistance of resistances  $0.2 \text{ } \Omega$ ,  $0.3 \text{ } \Omega$ ,  $0.4 \text{ } \Omega$ ,  $0.5 \text{ } \Omega$ , and  $12 \text{ } \Omega$ . These are connected in series. Hence, the sum of the resistances will give the value of  $R$ .

$$R = 0.2 + 0.3 + 0.4 + 0.5 + 12 = 13.4 \text{ } \Omega$$

Potential difference,  $V = 9 \text{ V}$

$$I = \frac{9}{13.4} = 0.671 \text{ A}$$

Therefore, the current that would flow through the  $12 \text{ } \Omega$  resistor is  $0.671 \text{ A}$ .

Question 10. How many  $176 \text{ ohm}$  resistors (in parallel) are required to carry  $5 \text{ A}$  on a  $220 \text{ V}$  line?

Answer:

For  $x$  number of resistors of resistance  $176 \text{ ohm}$ , the equivalent resistance of the resistors connected in parallel is given by Ohm's law as

$$V = IR$$

$$R = \frac{V}{I}$$

Where,

Supply voltage,  $V = 220 \text{ V}$

Current,  $I = 5 \text{ A}$

Equivalent resistance of the combination =  $R$ , given as

$$\frac{1}{R} = x \times \left( \frac{1}{176} \right)$$

$$R = \frac{176}{x}$$

From Ohm's law,

$$\frac{V}{I} = \frac{176}{x}$$

$$x = \frac{176 \times I}{V} = \frac{176 \times 5}{220} = 4$$

Therefore, four resistors of 176 ohm are required to draw the given amount of current.


Question 11. Show how you would connect three resistors each of resistance 6 ohm, so that the combination has a resistance of (i) 9 ohm, (ii) 4 ohm.

Answer:

If we connect the resistors in series, then the equivalent resistance will be the sum of the resistors, i.e., 6 ohm + 6 ohm + 6 ohm = 18 ohm, which is not desired. If we connect the resistors in parallel then the equivalent resistance will be

$\frac{6}{2} = 3 \Omega$ , which is also not desired. Hence, we should either connect the two resistors in series or parallel.

(i) Two resistors in parallel

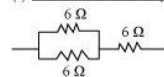


Two 6  $\Omega$  resistors are connected in parallel. Their equivalent resistance will be

$$\frac{1}{\frac{1}{6} + \frac{1}{6}} = \frac{6 \times 6}{6 + 6} = 3 \Omega$$

The third 6  $\Omega$  resistor is in series with 3  $\Omega$ . Hence, the equivalent resistance of the circuit is 6  $\Omega$  + 3  $\Omega$  = 9  $\Omega$ .

(ii) Two resistors in series

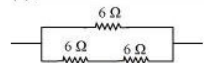

Two 6  $\Omega$  resistors are in series. Their equivalent resistance will be the sum 6 + 6 = 12  $\Omega$

The third 6  $\Omega$  resistor is in parallel with 12  $\Omega$ . Hence, equivalent resistance will be

$$\frac{1}{\frac{1}{12} + \frac{1}{6}} = \frac{12 \times 6}{12 + 6} = 4 \Omega$$

Therefore, the total resistance is 4  $\Omega$ .

Question 12. Several electric bulbs designed to be used on a 220 V electric supply line, are rated 10 W. How many lamps can be connected in parallel with each other across the two wires of 220 V line if the maximum allowable current is 5 A?

Answer:

$$P_1 = \frac{V^2}{R_1}$$

$$R_1 = \frac{V^2}{P_1}$$

Where,

Supply voltage,  $V = 220 \text{ V}$

Maximum allowable current,  $I = 5 \text{ A}$

Rating of an electric bulb  $P_1 = 10 \text{ W}$

$$R_1 = \frac{(220)^2}{10} = 4840 \Omega$$

According to Ohms law,

$$V = IR$$

Where,

$R$  is the total resistance of the circuit for  $x$  number of electric bulbs

$$R = \frac{V}{I} = \frac{220}{5} = 44 \Omega$$

Resistance of each electric bulb,  $R_1 = 4840 \Omega$

$$\therefore \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_1} + \dots \text{up to } x \text{ times}$$

$$\frac{1}{R} = \frac{1}{R_1} \times x$$

$$x = \frac{R_1}{R} = \frac{4840}{44} = 110$$

Therefore 110 electric bulbs are connected in parallel.

\*\*\*\*\* END \*\*\*\*\*